


Remind: Insertion Loss Method: Example 1

Design a filter with $\omega_c = 6 \text{ GHz}$, 15 dB attenuation at 8 GHz, $Z_o = 50 \Omega$, 3 dB equal ripple

$$z_o = 4.35 * 50 = 217.5 \Omega$$

$$z_o = 1.299 * 50 = 64.9 \Omega$$

$$z_o = 1.405 * 50 = 70.3 \Omega$$

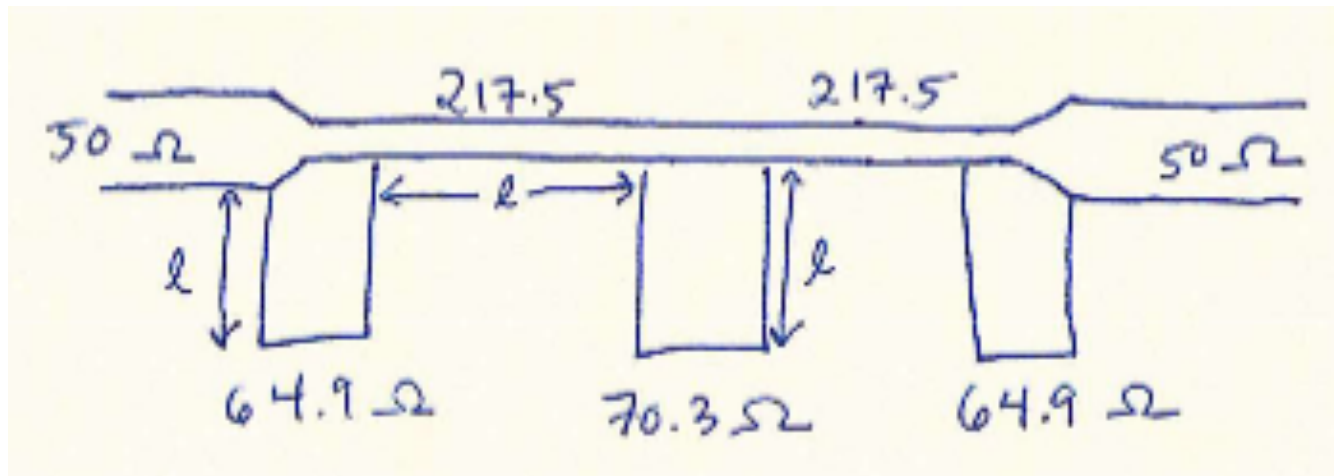


Remind: Insertion Loss Method: Example 1


- $\omega_c = 6 \text{ GHz}$, 3rd order, $Z_0 = 50 \Omega$, 3 dB equal ripple, 15 dB attenuation at 8 GHz

N	g ₁	g ₂	g ₃	g ₄	g ₅	g ₆	g ₇	g ₈	g ₉	g ₁₀	g ₁₁
1	1.9953	1.0000									
2	3.1013	0.5339	5.8095								
3	3.3487	0.7117	3.3487	1.0000							
4	3.4389	0.7483	4.3471	0.5920	5.8095						
5	3.4817	0.7618	4.5381	0.7618	3.4817	1.0000					
6	3.5045	0.7685	4.6061	0.7929	4.4641	0.6033	5.8095				
7	3.5182	0.7723	4.6386	0.8039	4.6386	0.7723	3.5182	1.0000			
8	3.5277	0.7745	4.6575	0.8089	4.6990	0.8018	4.4990	0.6073	5.8095		
9	3.5340	0.7760	4.6692	0.8118	4.7272	0.8118	4.6692	0.7760	3.5340	1.0000	
10	3.5384	0.7771	4.6768	0.8136	4.7425	0.8164	4.7260	0.8051	4.5142	0.6091	5.8095

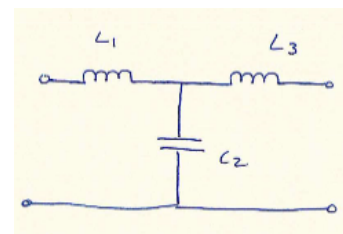
$$\begin{aligned} g_1 &= 3.3487 = L_1 \\ g_2 &= 0.7117 = c_2 \\ g_3 &= 3.3487 = L_3 \\ g_4 &= 1 = R_L \end{aligned}$$



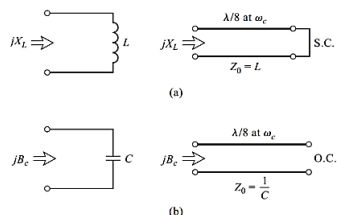Convert L's and C's to stubs:
using Richard's transformation





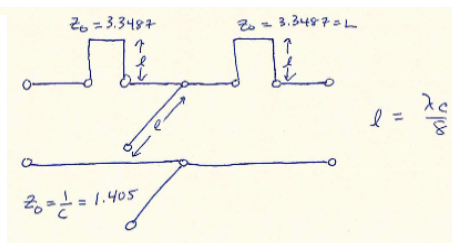Richards' transformation. (a) For an inductor to a short-circuited stub. (b) For a capacitor to an open-circuited stub.




Add unit elements at end of filter:
use Kuroda Identities

TABLE 8.7 The Four Kuroda Identities ($n^2 = 1 + Z_2/Z_1$)

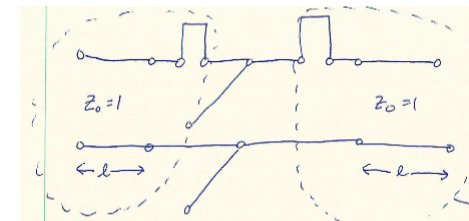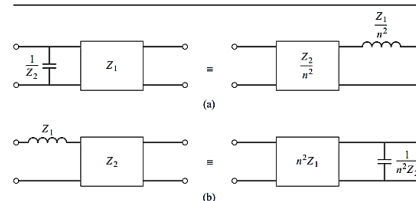

Replace with 2nd identity
 $Z_1 = 3.3487$
 $Z_2 = 1$
 $n^2 = 1 + \frac{Z_2}{Z_1} = 1.3$


Replace with identity or
using symmetry

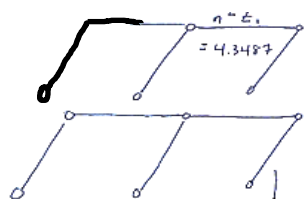

$$C = \frac{1}{n^2 Z_2} = 0.77 \Rightarrow \frac{1}{C} = 1.299$$

Impedance scale

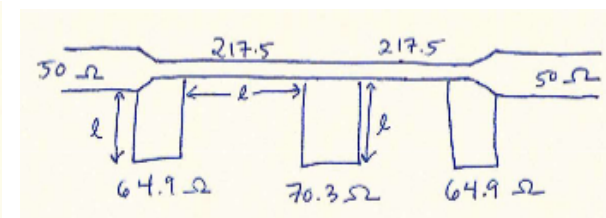
$$\begin{aligned} Z_0 &= 4.35 * 50 = 217.5 \Omega \\ Z_0 &= 1.299 * 50 = 64.9 \Omega \\ Z_0 &= 1.405 * 50 = 70.3 \Omega \end{aligned}$$



Insertion Loss Method LPF Sonnet Assignment

- Using the geometry obtained from the insertion loss LPF example 1, plot **S11** and **S22**
 - Cell size = 0.1×0.1
 - Box size = 30×30
 - Use Rogers 5880 ($\epsilon_r=2.2$ $d=1.5$ mm)

Sizes		X	Y	
Cell Size	0.1	0.1	<input type="checkbox"/> Lock	
Box Size	30.0	30.0	<input type="checkbox"/> Lock	
Num. Cells	300	300	<input type="checkbox"/> Lock	

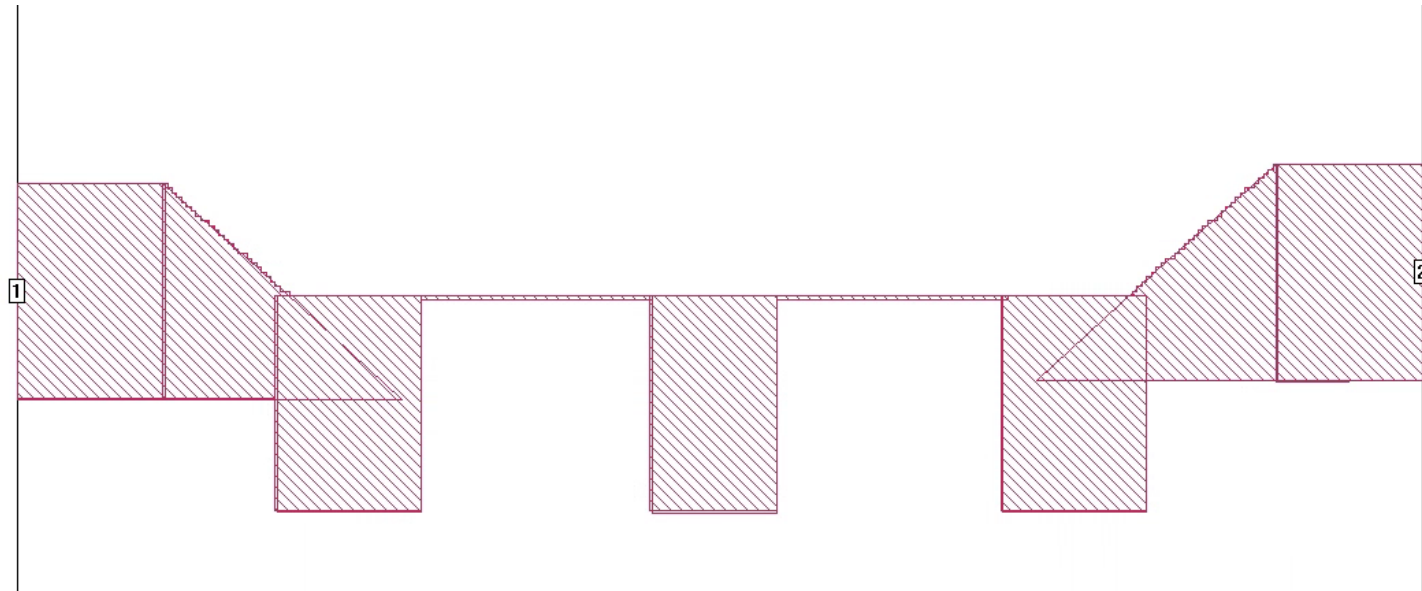



Insertion Loss Method LPF Assignment (Due April 20th Midnight Online Submission)

- Geometry

☐ Simulation Results (S11 and S21)

Discuss the simulation results

- 1.
- 2.
- 3.