

Example

Design an equal-split Wilkinson power divider for a $50\ \Omega$ system impedance at frequency f_0 , and plot the return loss (S_{11}), insertion loss ($S_{21} = S_{31}$), and isolation ($S_{23} = S_{32}$) versus frequency from $0.5f_0$ to $1.5f_0$.

Solution




From Figure 7.8 and the above derivation, we have that the quarter-wave transmission lines in the divider should have a characteristic impedance of

$$Z = \sqrt{2}Z_0 = 70.7\ \Omega,$$

and the shunt resistor a value of


$$R = 2Z_0 = 100\ \Omega.$$

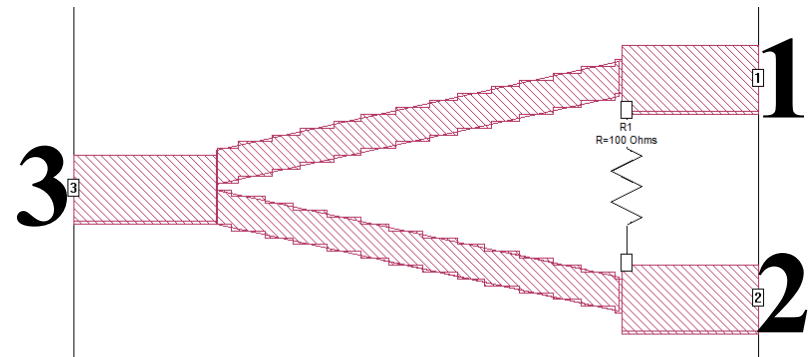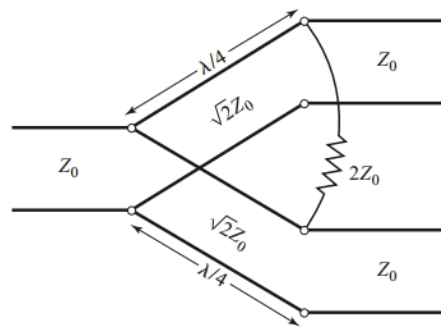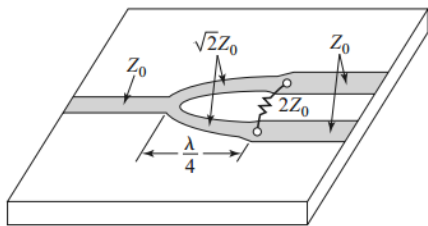The transmission lines are $\lambda/4$ long at the frequency f_0 . Using a computer-aided design tool for the analysis of microwave circuits, the scattering parameter magnitudes were calculated and plotted in Figure 7.12. ■






Wilkinson Power Divider Sonnet Assignment

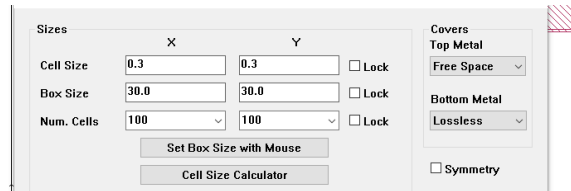- Using the Wilkinson Power Divider design in the example, obtain a plot for **S11, S22 and S33** and plot for **S21 and S31** using Sonnet.
 - Cell size = 0.3×0.3
 - Box size = 30×30
 - Use FR4 ($\epsilon_r=4.4$ $d=1.5$ mm)
 - Use “Rectangle” function to create the square geometry. “Edit points” feature can be used to move points as shown below.




Edit points

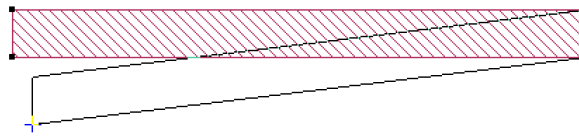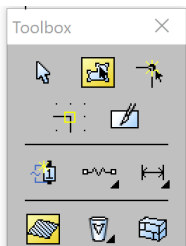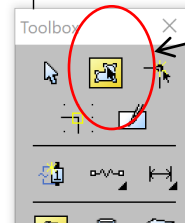

Click or drag to select point, drag to move them



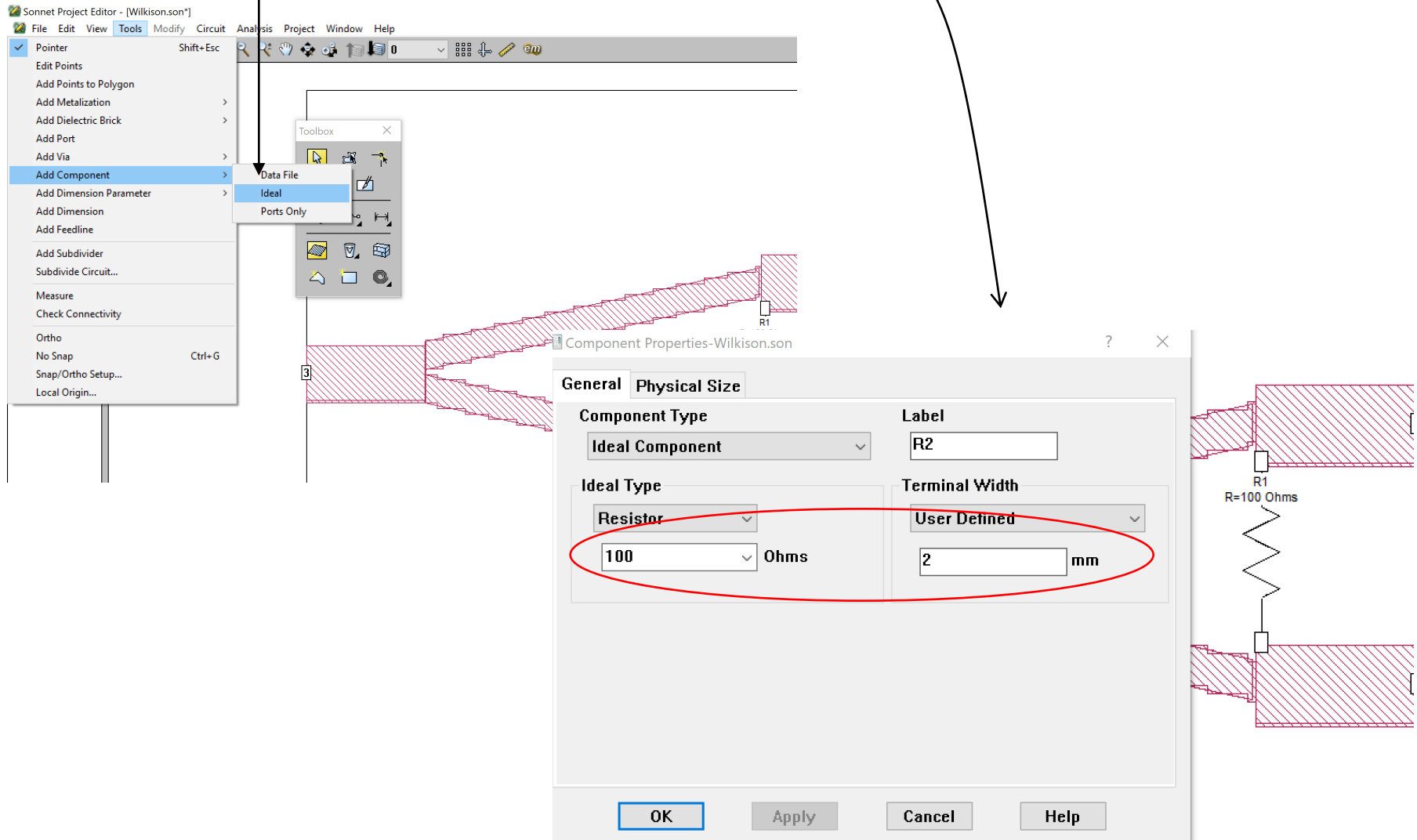- The resistor can be found under Tool → Add Component. Resistor properties should be set as shown below





Wilkinson Power Divider (Due April 20th Midnight Online Submission)

- Geometry

☐ **Simulation Results (S11, S22 and S33)**

☐ **Simulation Results (S21 and S31)**



Wilkinson Power Divider (Due April 20th Midnight Online Submission)

Discuss the simulation results

- 1.
- 2.
- 3.